



Transmission Line Topologies

-Baseline Board


ZhangHeng

Outline

- Baseline Board Overview
- Transmission Line Topologies
- Simulation Waveforms

Baseline Board Overview

 - 64 correlator chips
- 64 LTA controllers
- 64 DDR SDRAM (each LTA controller has 1)
- 16 recirculation controllers
- 32 dual-port static RAM (each recirculation controller has 2)
- 1 Gigabit Ethernet chip
- 1 decoder chip
- 1 PC104+ and PCMC mezzanine card
- 2 HM connectors
- 5V, 3.3V, 2.5V, 1.5V, 1.2V power supplies
- LEDs, switches, capacitors, resistors...




Transmission Line Topologies –

Recirculation Controller to Correlator Chip


- Data: 256 Mbits/sec
- Clock: 128 MHz
- Point-to-point bus chain
- 2.5V LVTTTL I/Os
- Clock has a series terminator

 Transmission Line Topologies – Recirculation Controller to Correlator Chip




Simulation Waveforms – Recirculation Controller to Correlator Chip

- Data (no termination)

 

Simulation Waveforms – Recirculation Controller to Correlator Chip

- Clock (series termination)

 


Transmission Line Topologies –

Recirculation Controller to DP-SRAMs


- Address and Data: 128 Mbits/sec
- Clock: 128 MHz
- Address 1-to-2 multi-drop
- Data and clock point-to-point
- 2.5V LVTTTL I/Os

 Transmission Line Topologies – Recirculation Controller to DP-SRAMs




Simulation Waveforms – Recirculation Controller to DP-SRAMs

- Address (1-to-2 no termination)

 


Simulation Waveforms – Recirculation Controller to DP-SRAMs

- Data (point-to-point no termination)

 

Simulation Waveforms – Recirculation Controller to DP-SRAMs

 - Clock (point-to-point series termination)




Transmission Line Topologies –

Correlator Chip to LTA Controller

- Data: 128 Mbits/sec
- Clock: 128 MHz
- Data and clock: point-to-point
- 2.5V LVTTTL I/Os


Simulation Waveforms – Correlator Chip to LTA Controller

- Data (point-to-point no termination)

 

Simulation Waveforms – Correlator Chip to LTA Controller

 - Clock (point-to-point series termination)




Transmission Line Topologies –

LTA Controller to DDR SDRAM

- Address and Data: 256 Mbits/sec
- Clock: 128 MHz
- All signals: point-to-point
- SSTL-2 Class 2 I/Os

Simulation Waveforms – LTA Controller to DDR SDRAM

 - Address, Data and Clock (point-to-point no termination)




Transmission Line Topologies –

LTA Controller to Gbit Ethernet Chip


- Command, Response, Frame, Data: 125 Mbits/sec
- Clock: 31.25 MHz
- Clock, Command: 1-to-8 multi-drop
- Data, Frame, Response: 8-to-1 multi-driver
- SSTL-2 Class 2 I/Os

 Transmission Line Topologies – LTA Controller to Gbit Ethernet Chip




Simulation Waveforms – LTA Controller to Gbit Ethernet Chip

 - Clock (1-to-8 multi-drop with series and parallel termination)




Simulation Waveforms – LTA Controller to Gbit Ethernet Chip

 - Command (1-to-8 multi-drop, series and parallel termination)



Simulation Waveforms – LTA Controller to Gbit Ethernet Chip

 
- Data (8-to-1 multi-driver, parallel termination on both ends)



Transmission Line Topologies – MCB Interface


- Control, Address, Data: 33 Mbits/sec
- Clock: 33 MHz
- Clock, Control, Address: 1-to-8 multi-drop
- Data: 1-to-8 and 8-to-1 multi-point
- SSTL-2 Class 2 I/Os

 Transmission Line Topologies – MCB Interface




Simulation Waveforms – MCB Interface

 - Clock (1-to-8 multi-drop, parallel termination)




Simulation Waveforms – MCB Interface

 - Control (1-to-8 multi-drop, parallel termination)




Simulation Waveforms – MCB Interface

 - Data (1-to-8, parallel termination on both ends)



Simulation Waveforms – MCB Interface

 - Data (8-to-1, parallel termination on both ends)



Summary

- Post-layout simulation on high-speed Gbits/sec signals
- Many PCB layers to route signal traces
- SMT components on both sides, have to use micro-via, blind via technologies
- Use 5mil 50-ohm traces for all signals